

# Problem Statement Day #1

Circuit Designing

Analog

IEEE - DELHI TECHNOLOGICAL UNIVERSITY

April 29, 2020

## Multivibrator Circuit

A *multivibrator circuit* is a circuit which switches its output between a "HIGH" state and a "LOW" state. How fast the state changes depends on the frequency of multivibrator. Another important parameter for this circuit is "Duty Cycle" which is defined as:

$$\text{Frequency } (\nu) = \frac{1}{t_{HIGH} + t_{LOW}}$$
$$\text{Duty Cycle} = \frac{t_{HIGH}}{t_{HIGH} + t_{LOW}} \cdot 100 \%$$

### Basic Principle

The circuit works by charging a capacitor  $C$  through a charging resistor  $R_{charging}$ . When the voltage across the capacitor reaches a certain threshold value *Threshold 1*, output state is inverted and the discharging circuit is switched on. Now, the capacitor is discharged through resistor  $R_{discharging}$ . When voltage across capacitor reaches lower threshold value *Threshold 2*, output state is again inverted, and the charging circuit is switched on. Both circuits will have different value of time constants, and hence will determine the time to rise/sink to respective threshold value. This time will determine the frequency of the *multivibrator circuit* and its duty cycle:

$$\text{Frequency } (\nu) = \frac{1}{t_{T1} + t_{T2}}$$
$$\text{Duty Cycle} = \frac{t_{T1}}{t_{T1} + t_{T2}} \cdot 100 \%$$

where,  $t_{T1}$  is time to reach *Threshold 1* and  $t_{T2}$  is time to reach *Threshold 2* from *Threshold 1*.

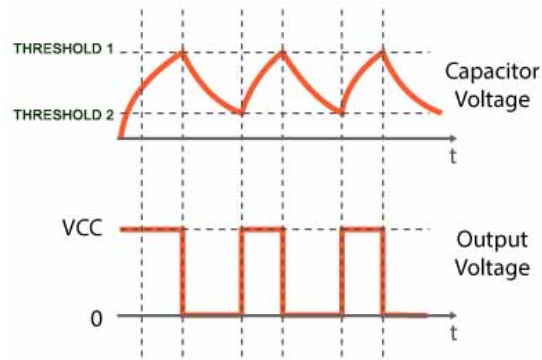


Figure 1: Waveform of Capacitor voltage (above) and corresponding Square Wave output (bottom)

### Problem Statement

A *multivibrator circuit* is used to generate high frequency square wave. Design a *multivibrator circuit* using principles described above, and generate a square wave of 41 kHz.

### Additional Information

- Highlight the charging resistor (using name `R_charging`), the discharging resistor (using name `R_discharging`), and the capacitor (using name `C_t`).
- Use of Pulse Voltage Source is not allowed. Use of behavioral digital components from LTSpice is NOT allowed.
- Output voltage is  $V_{pp} = 5V$ .
- Waveform of output square wave, and of voltage across capacitor `C_t` will be used to evaluate points for output (You should get a waveform similar to Fig. 1).
- Also give the formula for frequency and duty cycle of output square wave, as a function of `R_charging`, `R_discharging` and `C_t` in your report. Also give a short explanation on how you derived this expression.
- Keep checking the website for design tips.

### Optional

Frequency of output square wave needs to be changed according to analog input (0 – 5V). Input of 2.5V corresponds to 0 shift in frequency. Voltage of 0V/5V corresponds to +/- 1 kHz shift in frequency (keeping duty cycle constant while changing frequency is not necessary). Design a circuit (or modify the one you designed) to do so.